



*Department of Computer Science*  
University of Massachusetts,  
Amherst



# Moo 1.0 – A UMass Version Wireless Identification Sensing Platform



Hong Zhang  
Lab of PRISMS, Department of Computer Science,  
University of Massachusetts, Amherst

# Contents


- ❖ 1. How does Moo 1.0 work?
- ❖ 2. What are Moo 1.0' kernels?
- ❖ 3. What will do in the future?

# Contents

- ❖ 1. How does Moo 1.0 work?
- ❖ 2. What are Moo 1.0 kernels?
- ❖ 3. What can do in the future?


# 1. How does Moo 1.0 work?

## ❖ Block Diagram

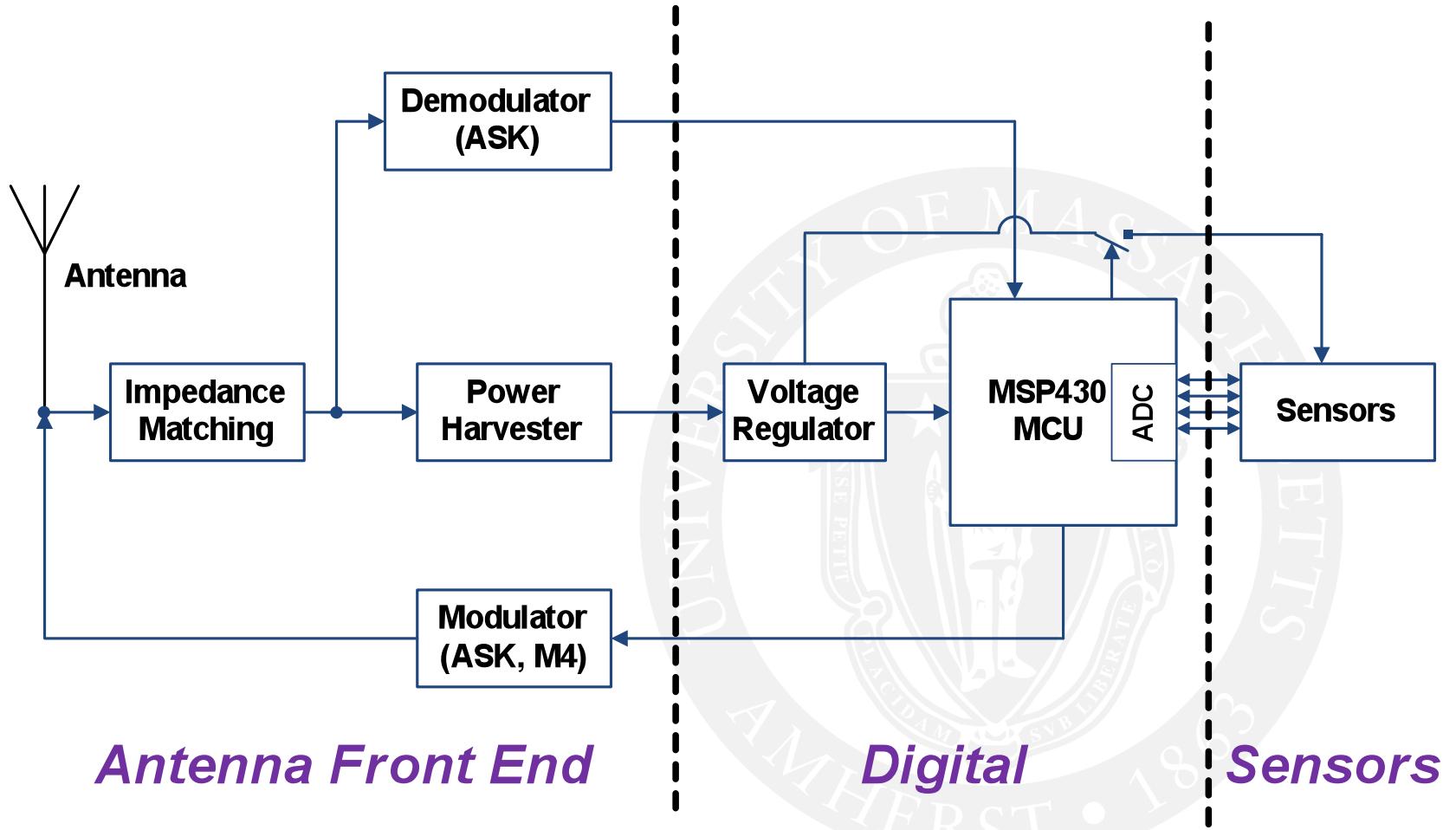


# 1. How does Moo 1.0 work?

## ❖ Impedance Matching

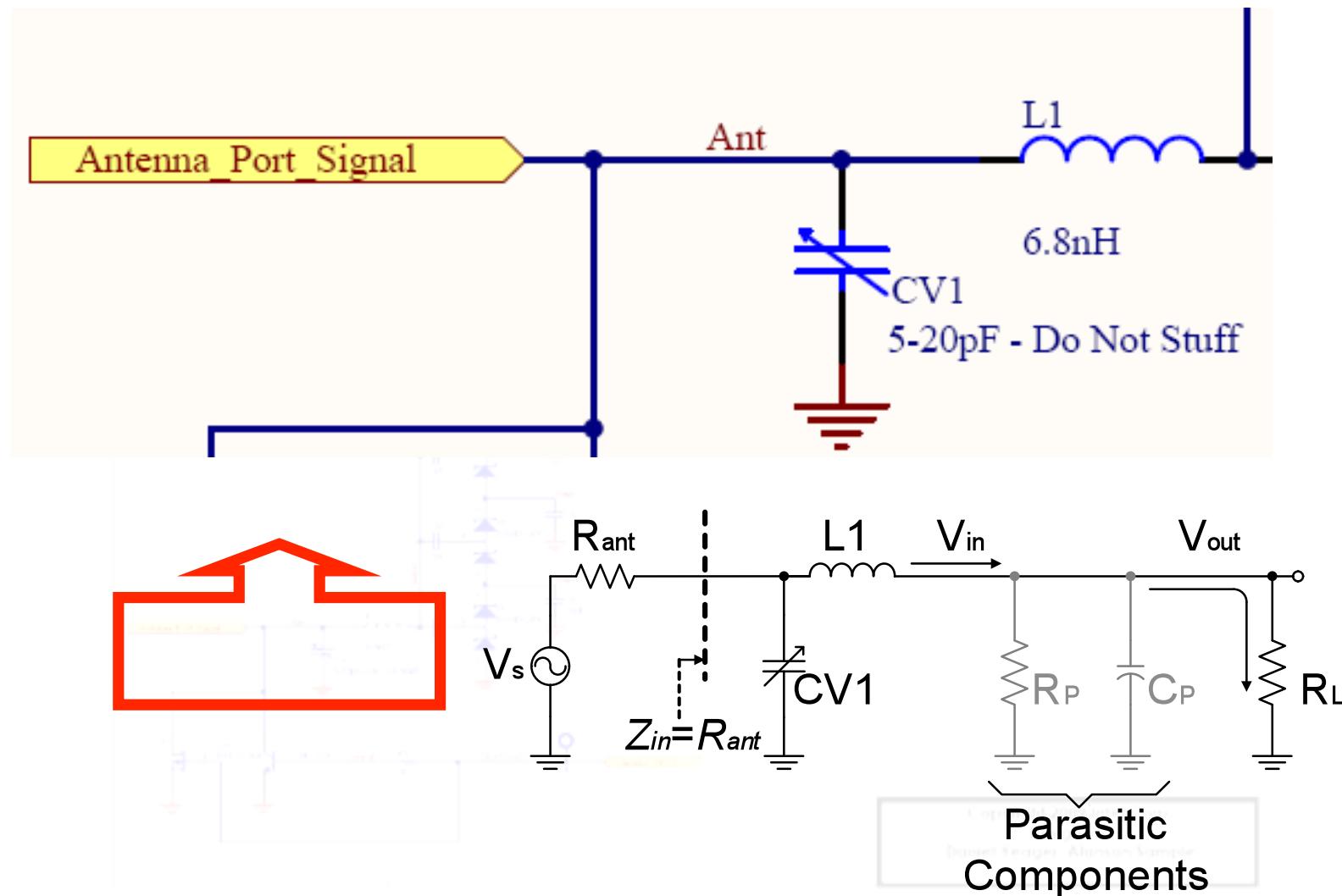


# 1. How does Moo 1.0 work?

## ❖ Power Harvester

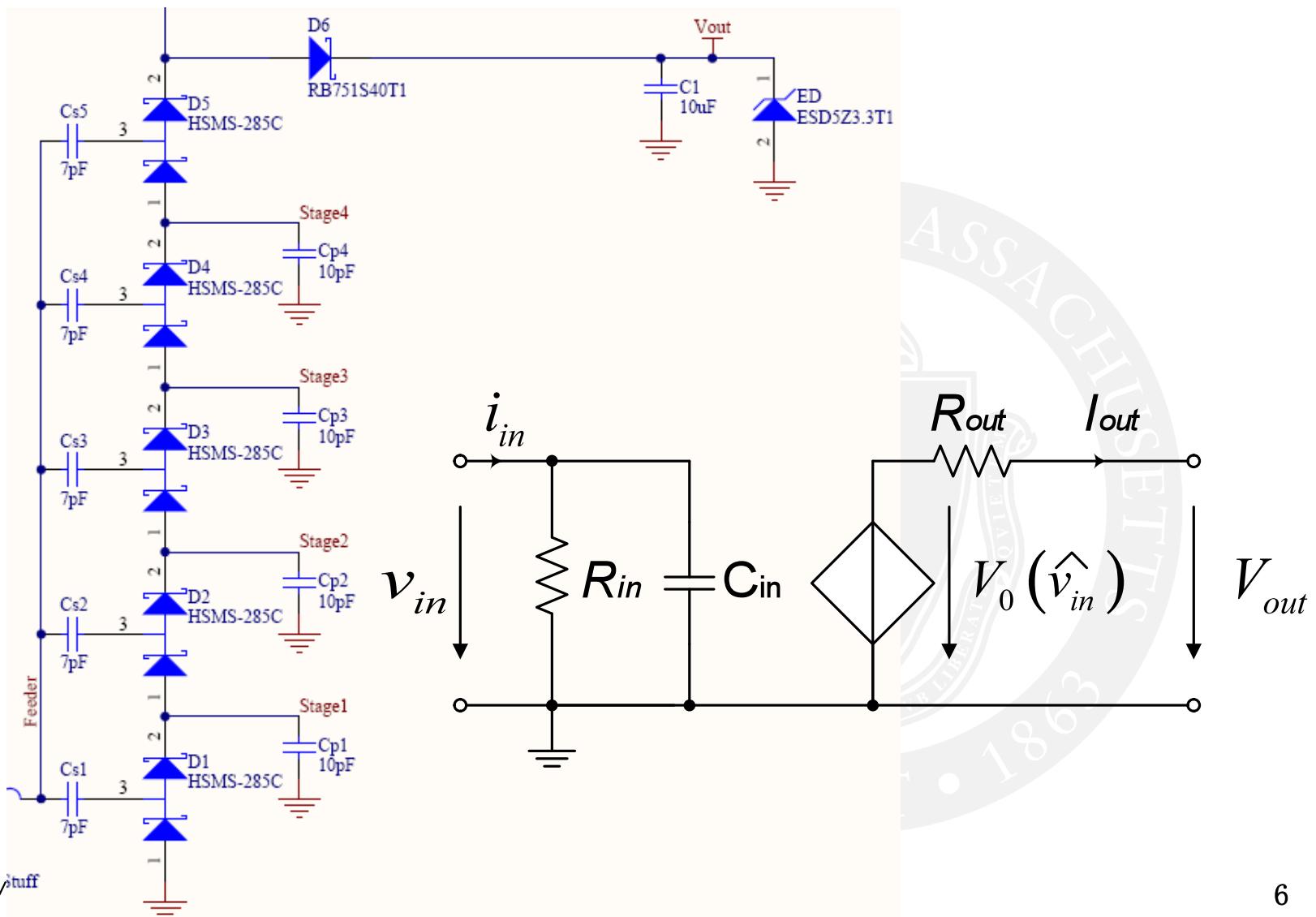

# 1. How does Moo 1.0 work?

## ❖ Power Harvester

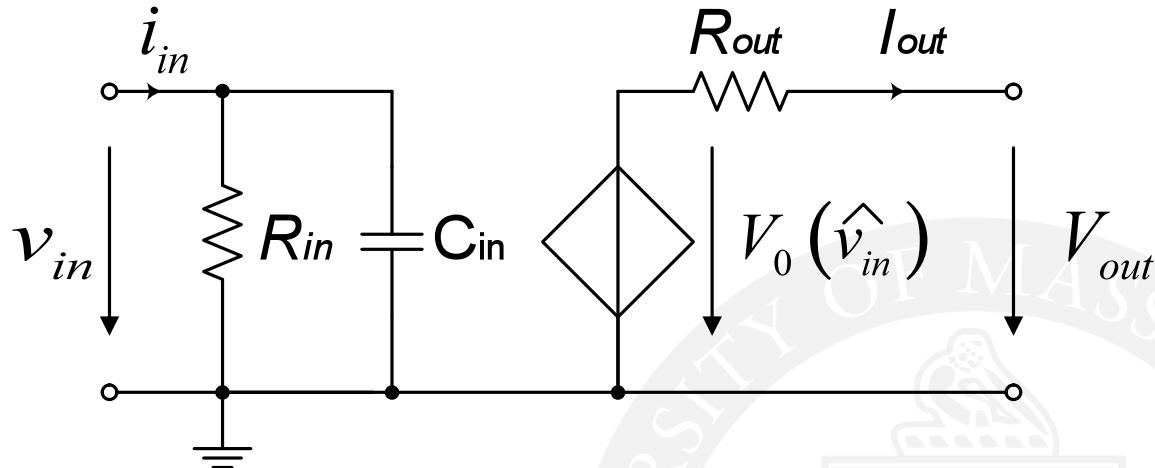

$$V_{out} = 2N\overline{V_D}, N = 5, \overline{V_D} \leq \hat{v}_{in}$$



$$R_{in} = \frac{\hat{v}_{in}}{4NI_{out}}, \text{ if } \overline{V_D} = \hat{v}_{in}$$

$$R_{out} = \frac{V_0 - V_{out}}{I_{out}}, V_0 = 2N\overline{V_D} \Big|_{I_{out}=0}$$

$$C_{in} = C_{in,rectifier} + C_{added}$$


# 1. How does Moo 1.0 work?
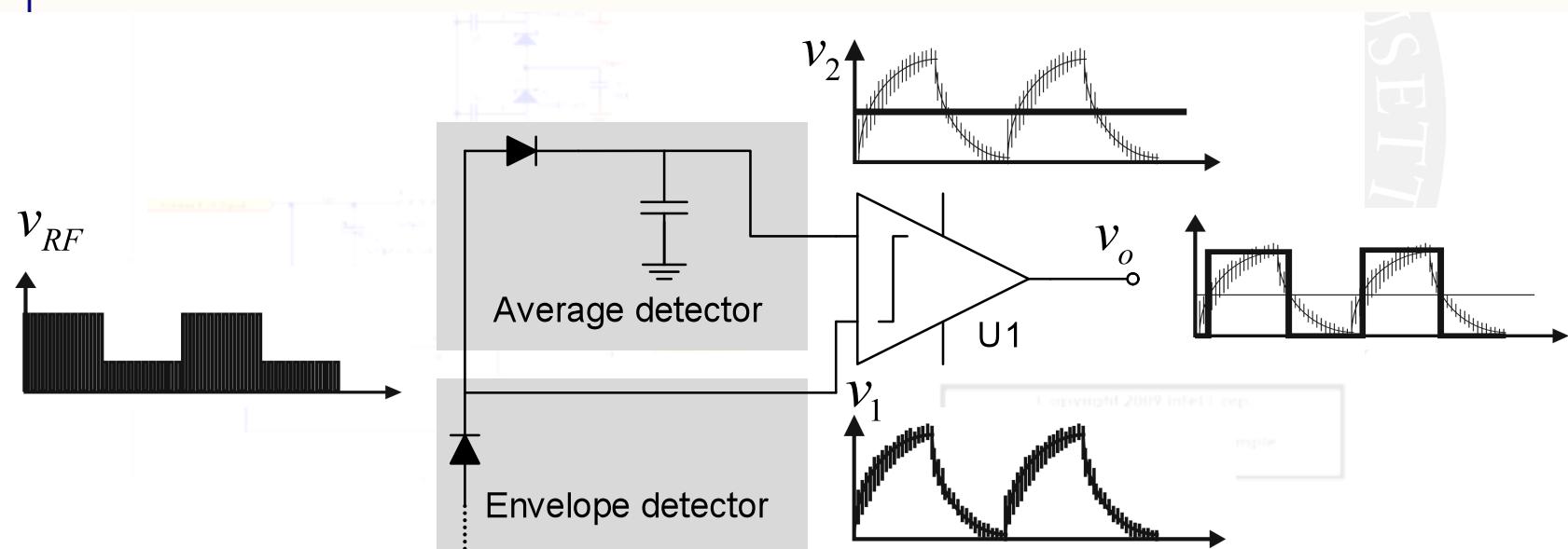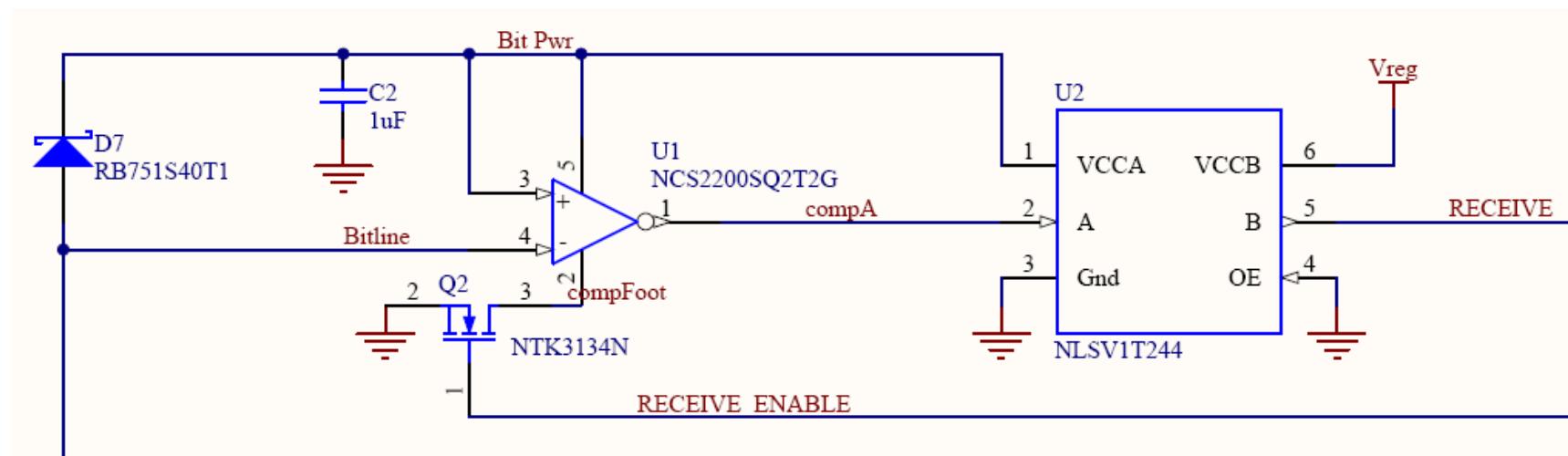
## ❖ Demodulator (ASK – Amplitude-Shift Keying)



# 1. How does Moo 1.0 work?
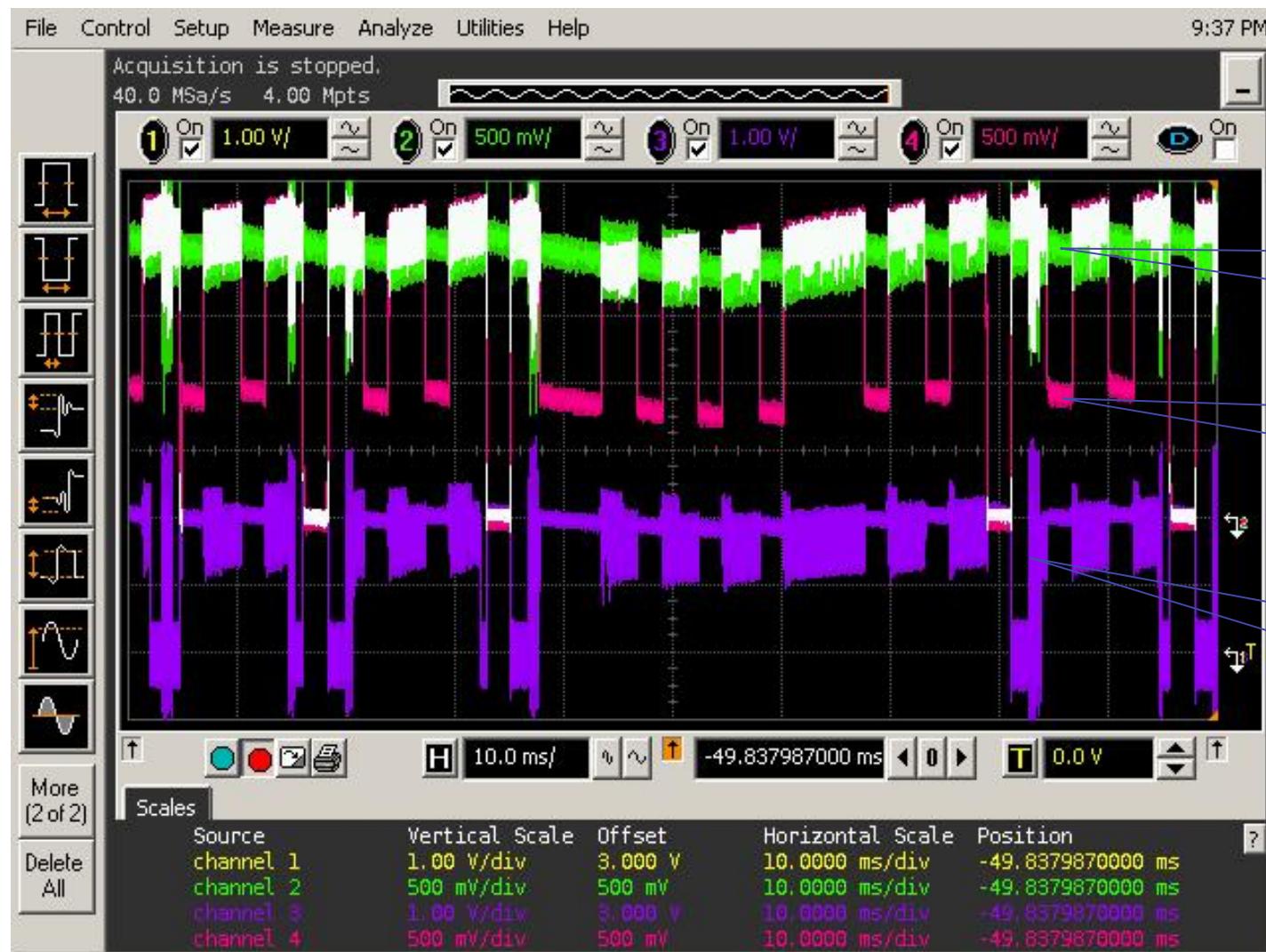
## ❖ Demodulator (ASK – Amplitude-Shift Keying)





Green: Bit Power

Pink: Bit Line

Purple: CompA




# 1. How does Moo 1.0 work?

## ❖ Voltage Regulator

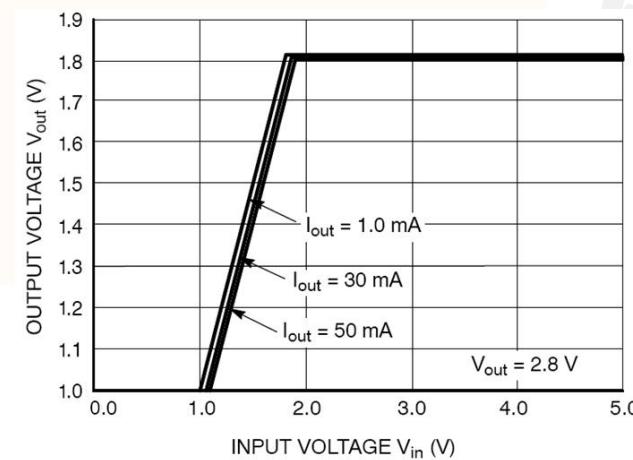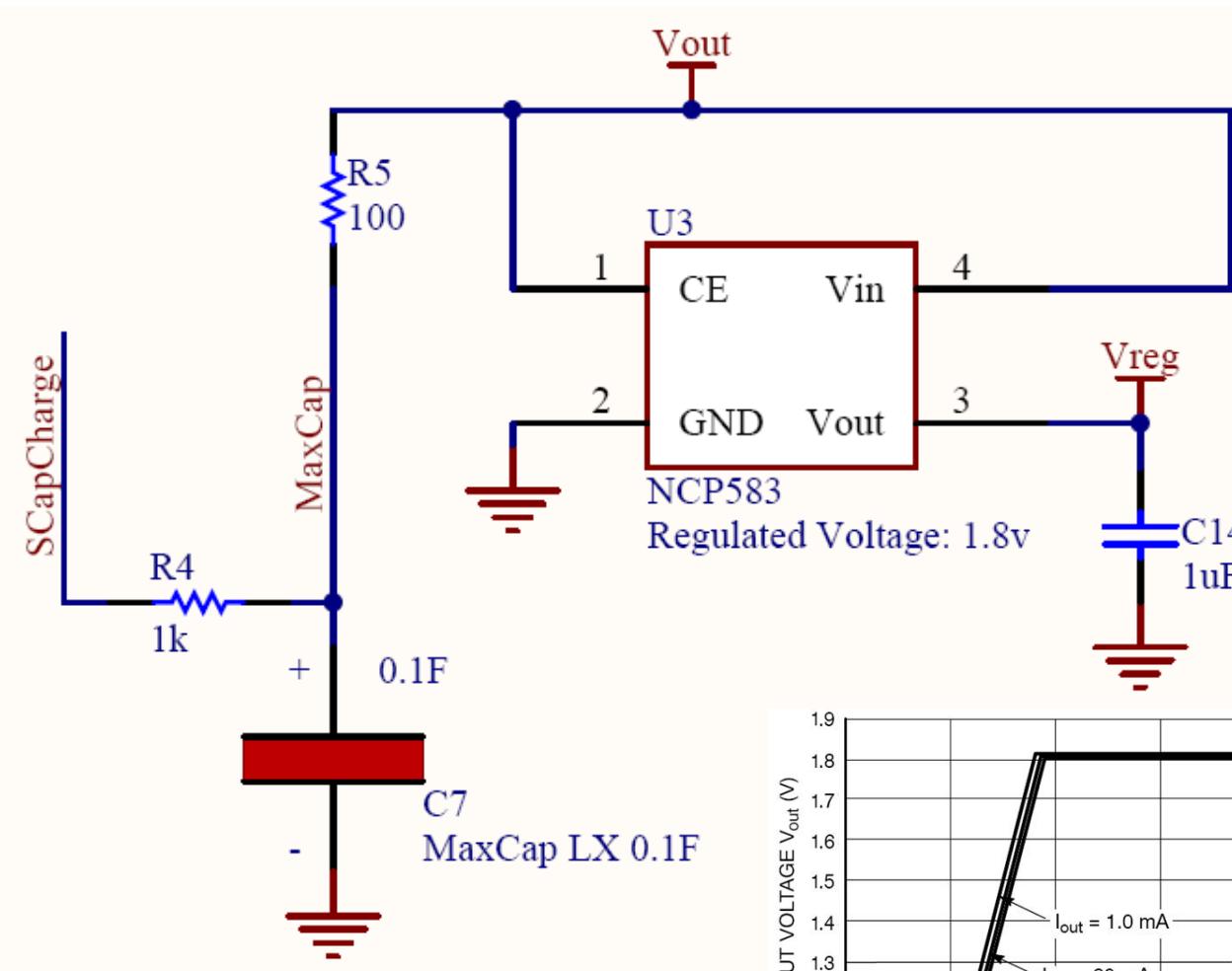


# 1. How does Moo 1.0 work?

## ❖ MSP430 Micro-Controller

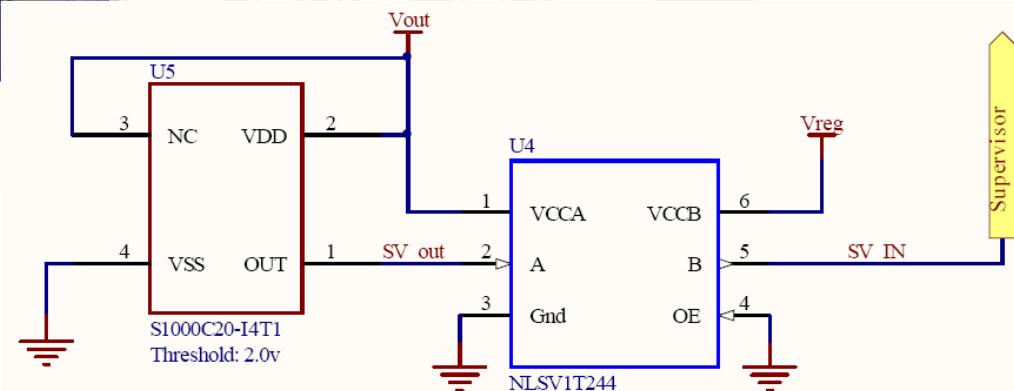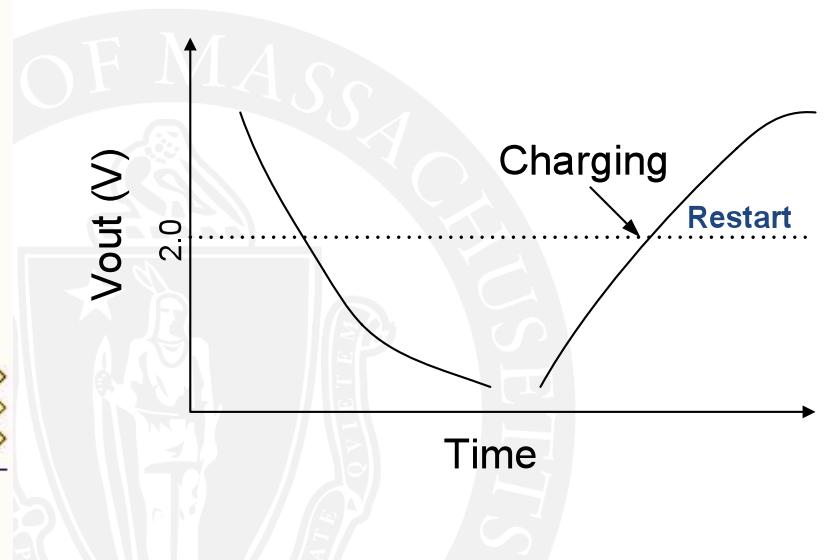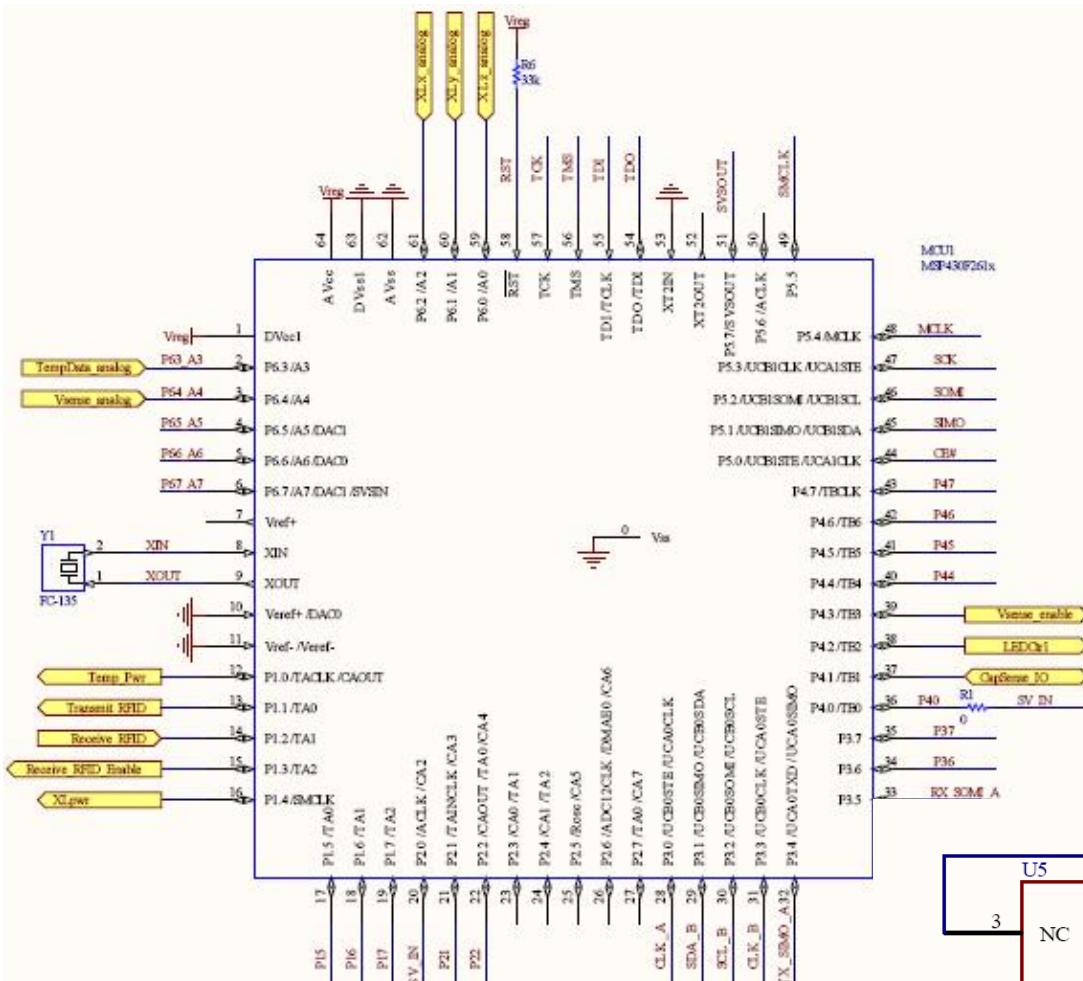


# 1. How does Moo 1.0 work?

## ❖ Sensors

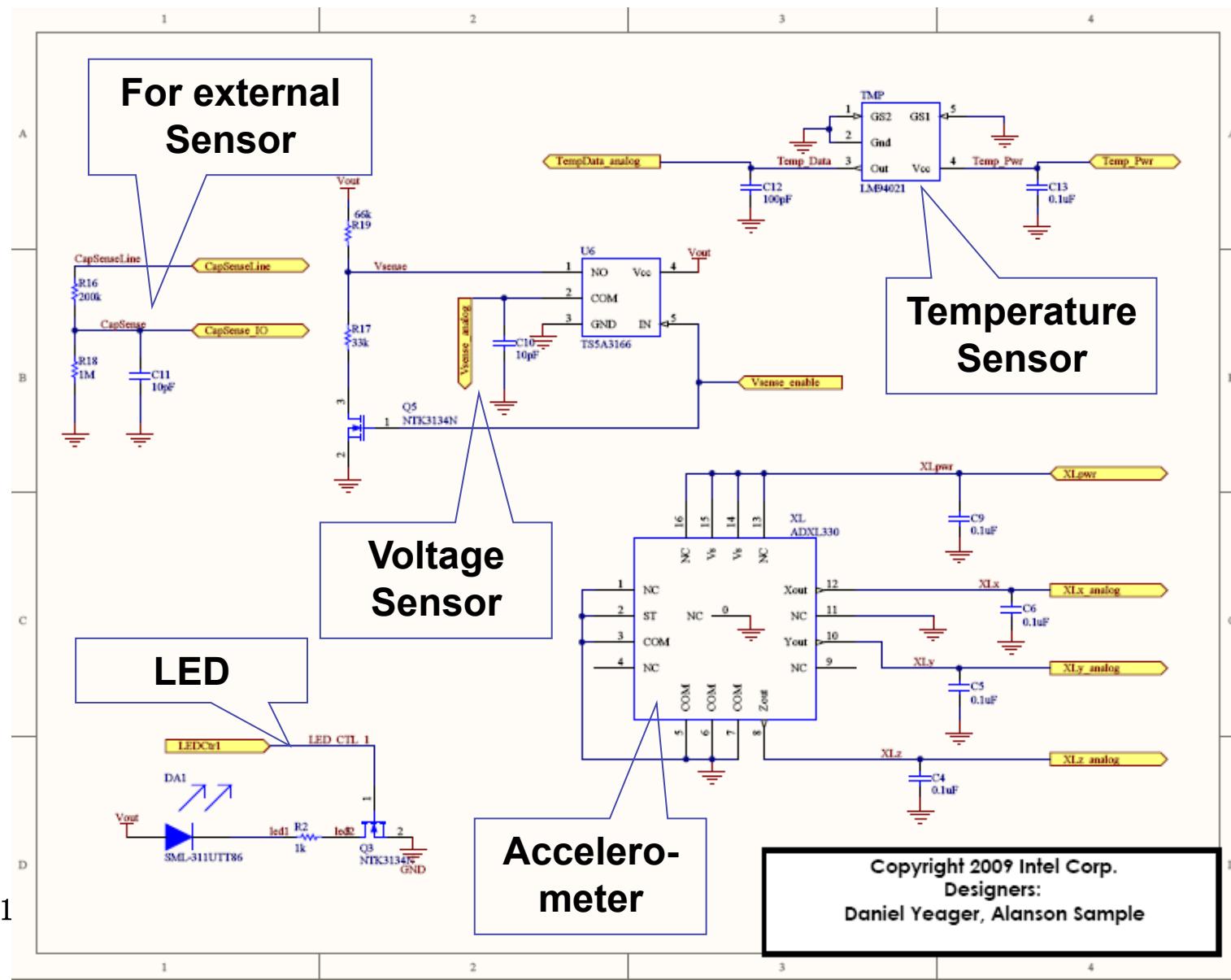

# 1. How does Moo 1.0 work?

## ❖ Modulator (ASK, M=4)

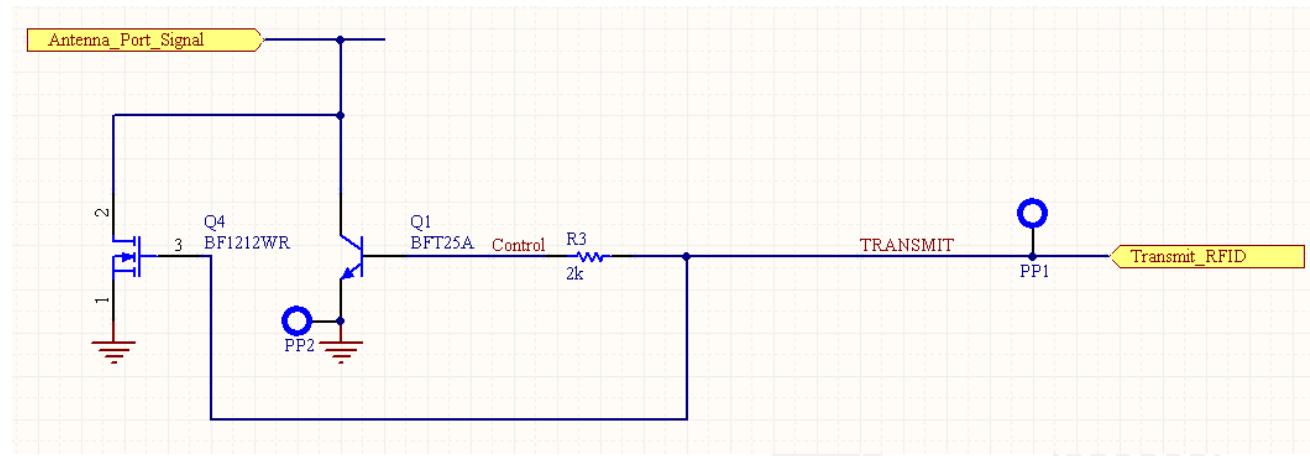

Miller Preamble (TRext = 1)



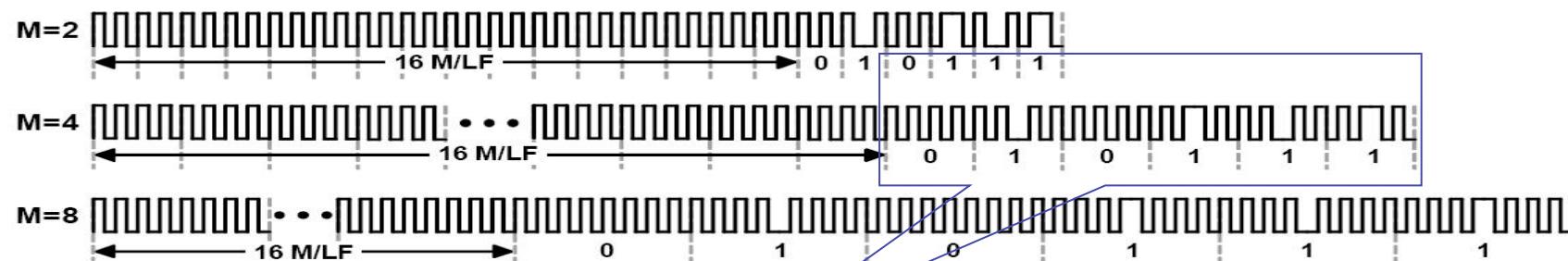


Figure 6.15 – Subcarrier T=>R preamble

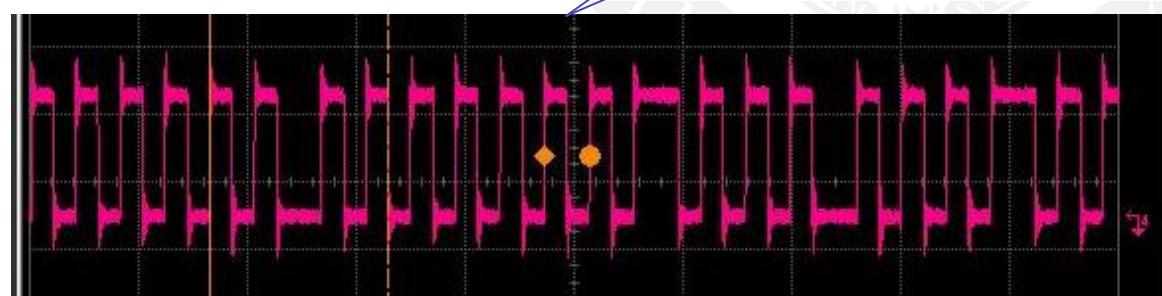
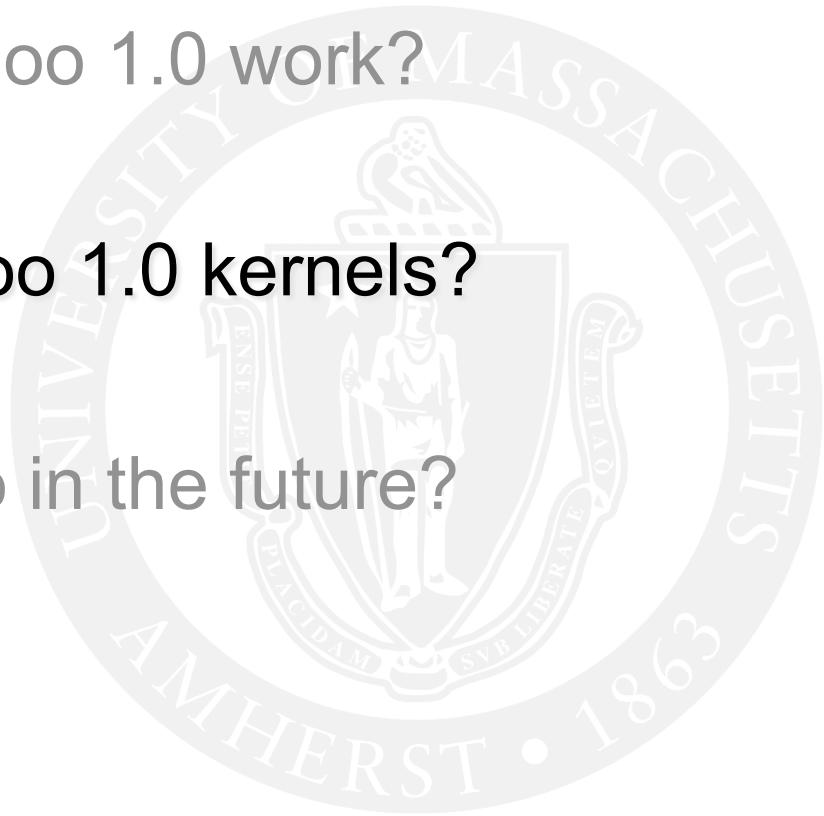
# Contents

- ❖ 1. How does Moo 1.0 work?
- ❖ 2. What are Moo 1.0 kernels?
- ❖ 3. What can do in the future?



## 2. What are Moo 1.0 kernels?

### ❖ MCU: MSP430F2618

MCU		MSP430F2618
Package		64-PIN QFP
Memory	Flash	<b>116KB+256B</b>
Size	RAM	<b>8KB</b>
	Supply Voltage	1.8V to 3.6V
Power Consumption	Active Mode	365uA@1MHz, 2.2V
	Standby Mode	<b>0.5uA</b>
	Off Mode	0.1uA
Architecture		16-Bit RISC Architecture 62.5ns Instruction Cycle Time 32-kHz Crystal 12-bit ADC/DAC
ADC	Supply Voltage	2.2V ~ 3.6V
	Supply Current	0.65mA@2.2V, 0.8mA@3V

## 2. What are Moo 1.0 kernels?


---

### ❖ Memory: External Flash

Type #	SST25WF040
Description	On Moo 1.0
Memory Size	<b>4M (512K x 8)</b>
Speed	<= 20MHz
Supply Voltage	<b>1.65v ~ 1.95v</b>
Active Current	2mA @ 20MHz
Standby Current	2uA
Interface	SPI Compatible: Mode 0 and Mode 3
R/W/E time	Byte program (Byte Write): 50us Chip-erase: 125ms Block-erase: 62ms
Package	8-lead SOIC (150 mils)
Size	LxW = 5.80mm x 5.00mm
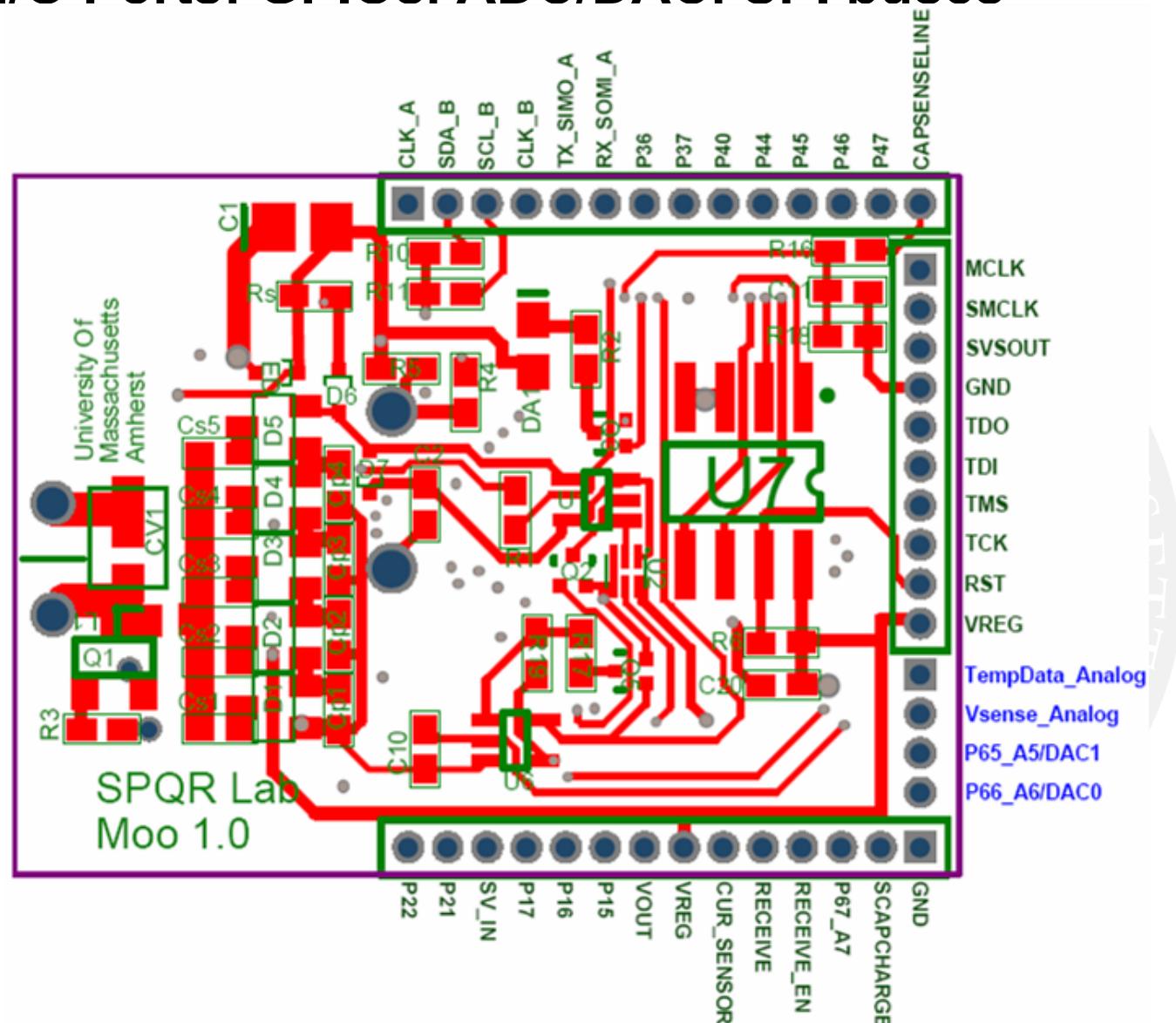
## 2. What are Moo 1.0 kernels?


- ❖ 42 I/O Ports: GPIOs. ADC/DAC. SPI buses


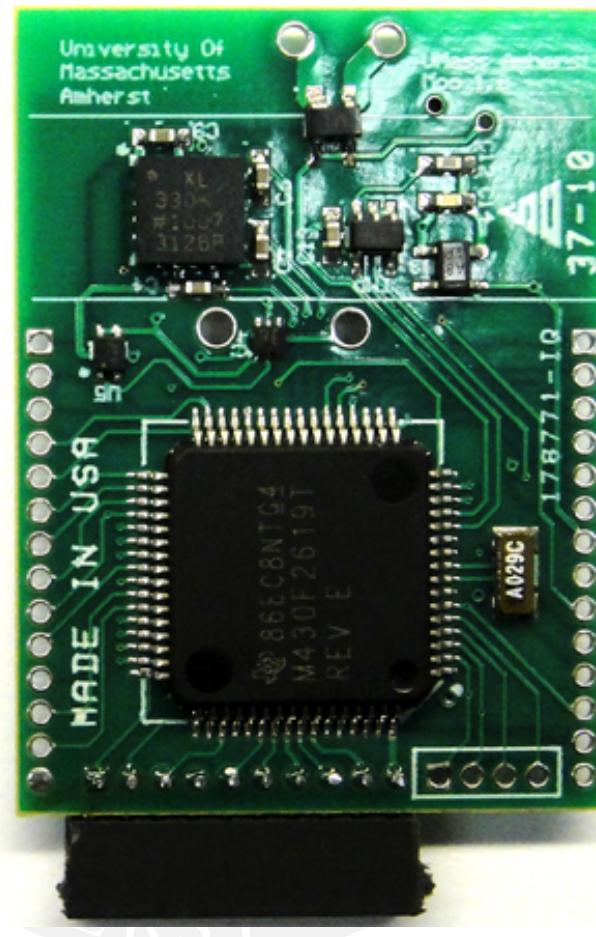
## 2. What are Moo 1.0 kernels?

---

- ❖ Size: Moo 1.0 vs a quarter dollar coin



## **2. What are Moo 1.0 kernels?**

---

### **❖ Some estimation about power consumptions**

- When Moo 1.0 is about 1.3ft from RFID reader, the power harvester can harvest about  $(3V)^2/(12.65k\Omega) = 0.7mW$ . The current is about 237uA.
- When the 10uF capacitor is fully charged, it has a voltage of about 5.4V. Before the voltage of it drops to 3V, it can provide  $(5.4^2-3^2)/2*10^{-5} = 0.1mJ$
- When Moo 1.0 works actively and ADC is converting, the power consumed is about  $3V*(365\mu A+0.8mA) = 3.5mW$
- With a full charged capacitor and harvesting from RFID reader at 1.3ft above, a rough estimation of continuous work time of Moo 1.0 is:  $0.1mJ/(3.5mW-0.7mW)=35.7ms$
- Without harvesting, the work time is:  $0.1mJ/3.5mW = 28.6ms$

# Contents

- ❖ 1. How does Moo 1.0 work?
- ❖ 2. What does Moo 1.0 improve?
- ❖ 3. What can do in the future?

### 3. What can do in the future?

- ❖ Antenna shape
  - Dipolar vs Meander

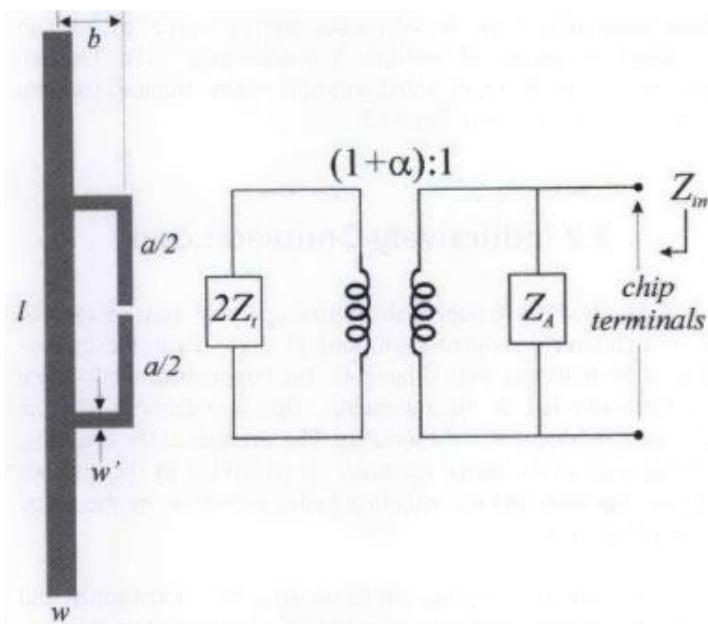


Figure 1. The T-match configuration for planar dipoles and the equivalent circuit, where the impedance step-up ratio  $(1+\alpha)$  is related to the conductors' cross sections.

5/19/11

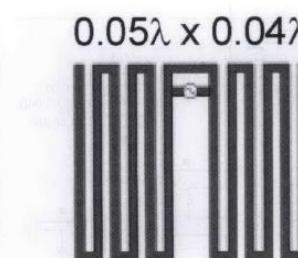


Figure 9a. An equi-spaced meander-line antenna.

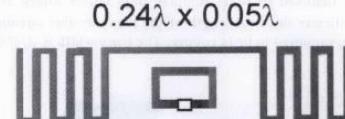


Figure 9b. A meander-line antenna with an inductively coupled loop feed.

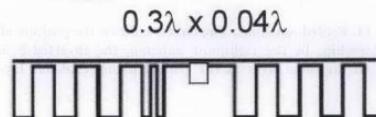


Figure 9c. An equi-spaced meander-line antenna with a loading bar.

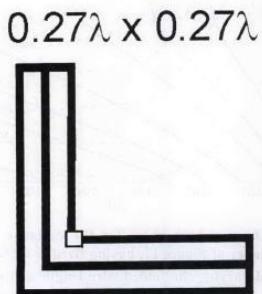


Figure 9d. A doubly-folded L-shaped dipole.

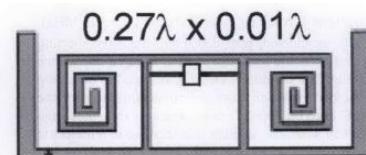


Figure 9e. A multiconductor antenna with a double T-match scheme and spiral folding.

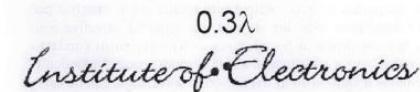


Figure 9f. A text-shaped meander-line antenna.

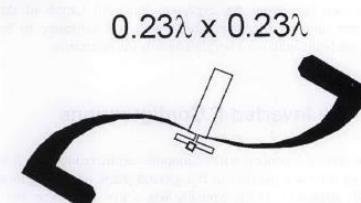


Figure 9g. A resonant tapered dipole that is partially meandered, with a resistive shorting stub and a double inductive stub.


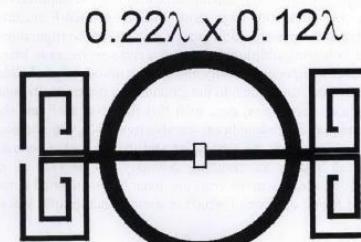


Figure 9h. A multiconductor meander-line tag with a circular-shaped double T-match.


### 3. What can do in the future?

#### ❖ Regulator

- Linear vs Switch

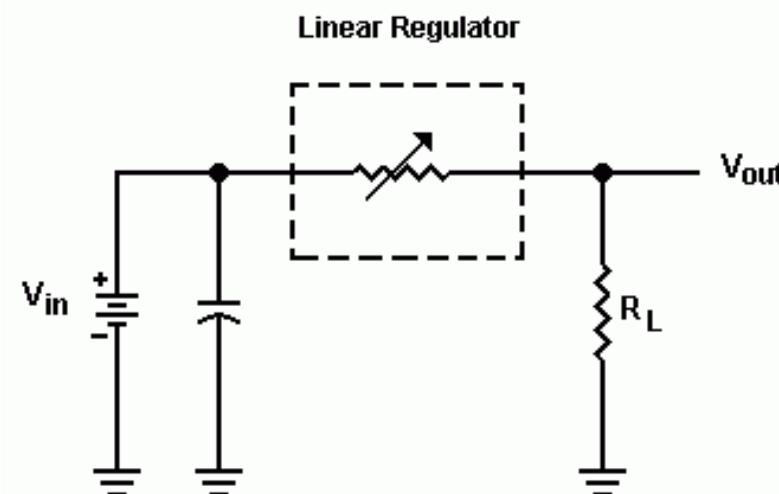

Switching Regulator

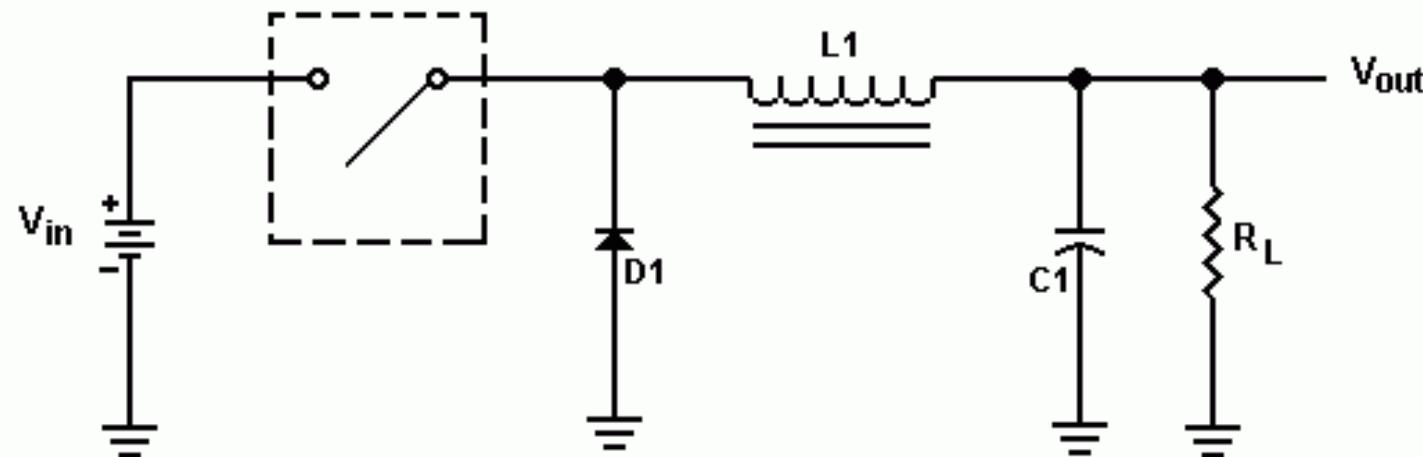

### **3. What can do in the future?**

---

- ❖ **Adaptive firmware**
  - **Mementos**
  - ...



# Thanks!

